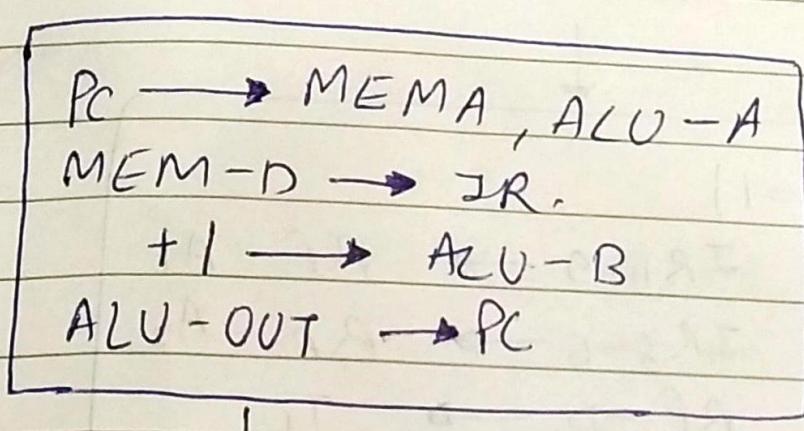
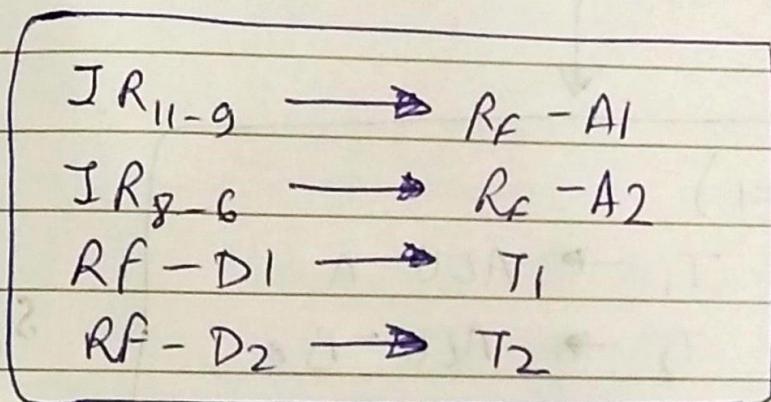
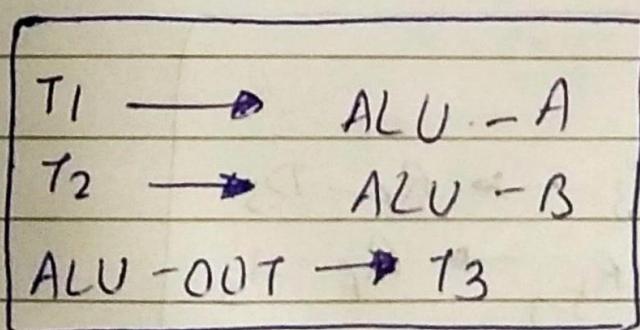
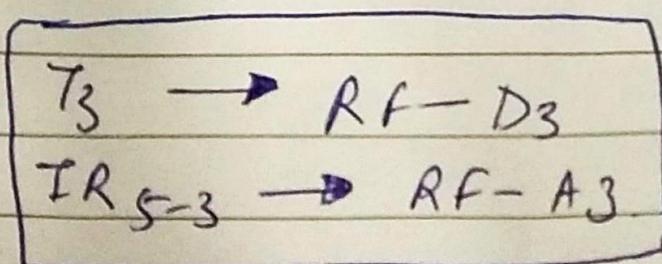


EE 224 Project

Names :-

- 1) Ashish Prasad (21D180009)
- 2) Aarushi Agrawal (21D070003)
- 3) Pradyuman Agrawal (210020090)
- 4) Prajapati Kishan K (21D070048)

1. ADD RC, RA, RB / 5. NDU Rc, Rn, RB

S₁S₂S₃S₄

2. ADC RC, RA, RB / 6. NDC RC, RA, RB

S₁



IF (C=1)

IR₁₁₋₉ → RF - A₁

IR₈₋₆ → RF - A₂

RF - D₁ → T₁

RF - D₂ → T₂

S₅



IF (C=1)

T₁ → ALU - A

T₂ → ALU - B

ALU - OUT → T₃

S₆



IF (C=1)

T₃ → RF - D₃

IR₅₋₃ → RF - A₃

S₇

8. $AD \in R_C, R_A, R_B$ | 7. $ND \in RA, RB, PC$

S_1



IF ($Z = 1$)


$IR_{11-9} \rightarrow RF - A_1$

$IR_{8-6} \rightarrow RF - A_2$

$RF - D_1 \rightarrow T_1$

$RF - D_2 \rightarrow T_2$

S_8

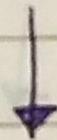

IF ($Z = 1$)

$T_1 \rightarrow ALU - A$

$T_1 \rightarrow ALU - B$

$ALU-OUT \rightarrow T_3$

S_9



IF ($Z = 1$)


$T_3 \rightarrow RF - D_3$

$IR_{5-3} \rightarrow RF - A_3$


S_{10}

4. ADI RB, RA, IMM6


S_1

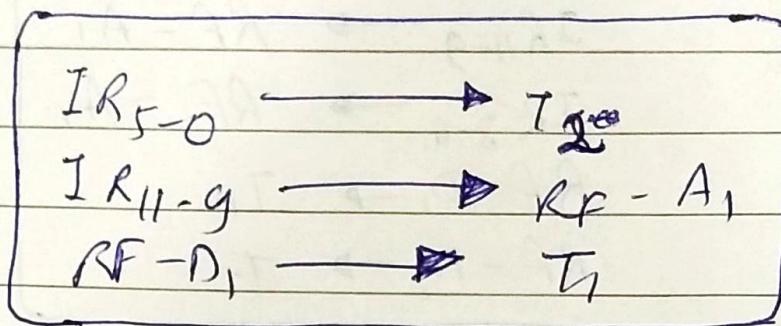

S_{11}






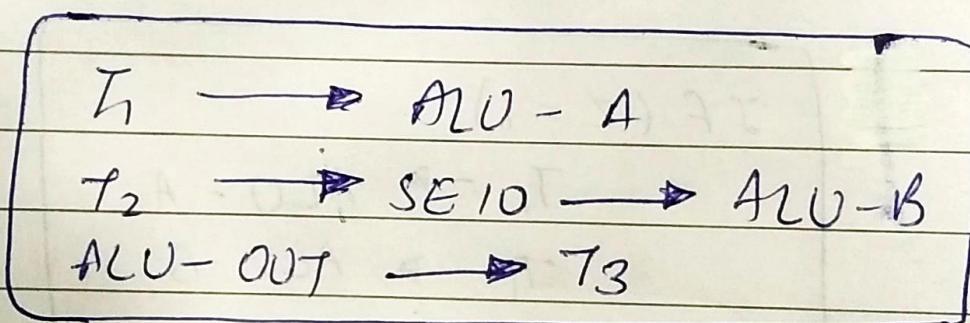


S_{12}

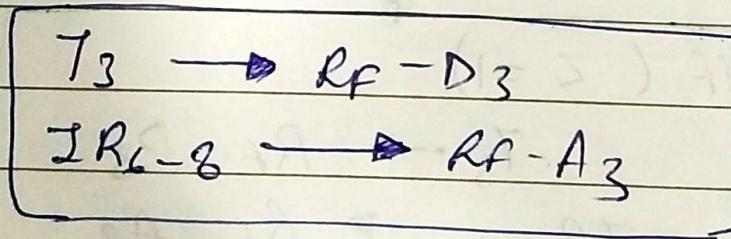


S_{13}


8-

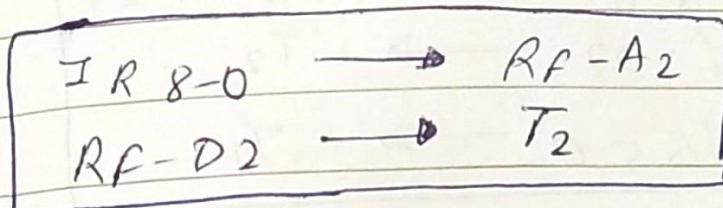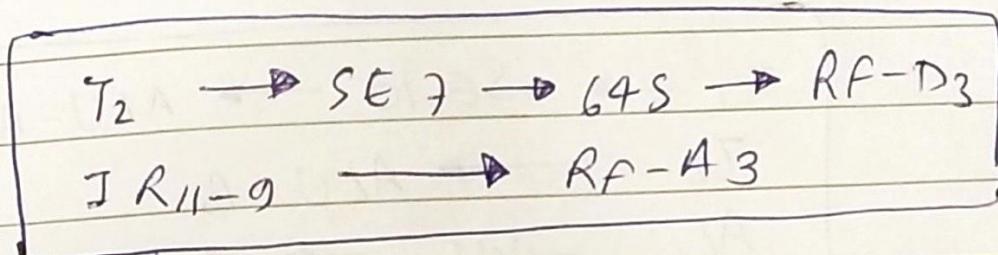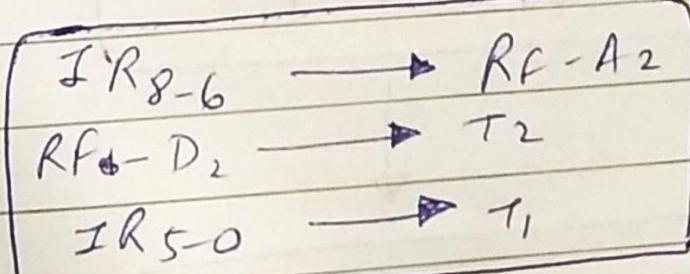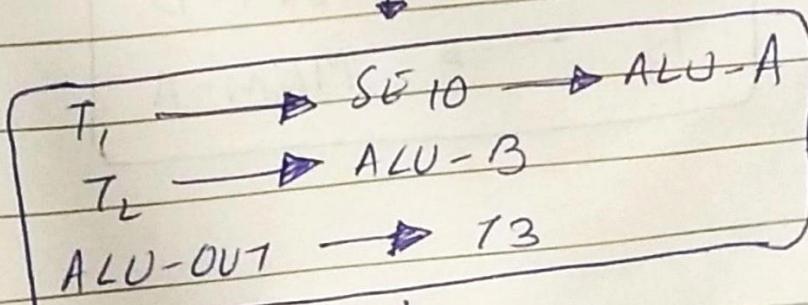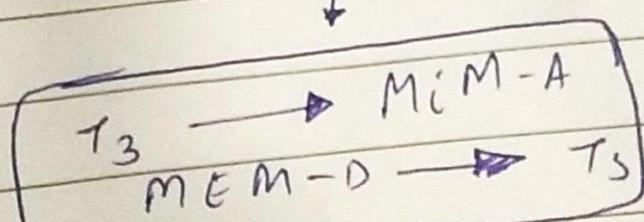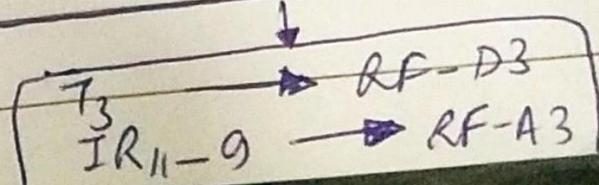LHI RA, JAMMS₁S₁₄S₁₅9. LW RA, RB, IMMS₁S₁₆S₁₇S₁₈S₁₉


10. SW RA, RB, IMM.

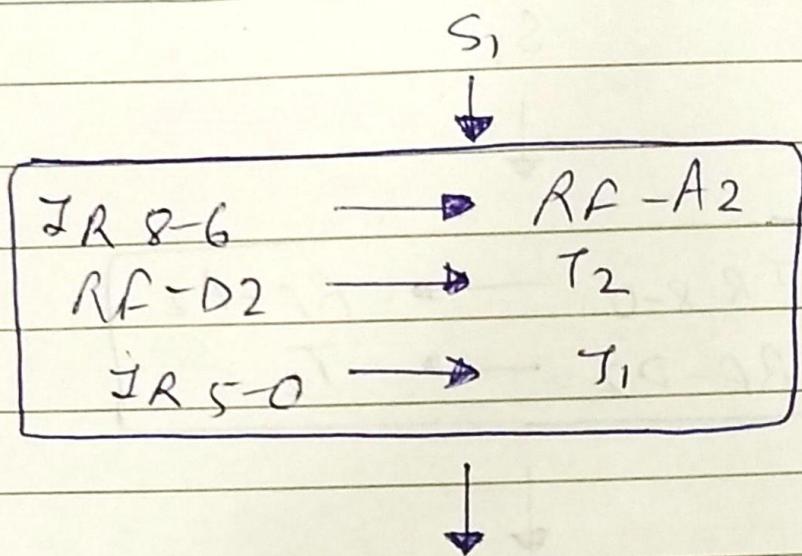


S_{16}

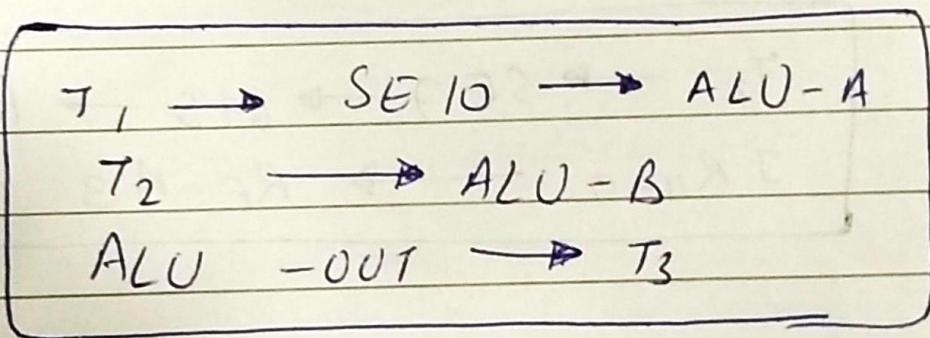


S_{17}

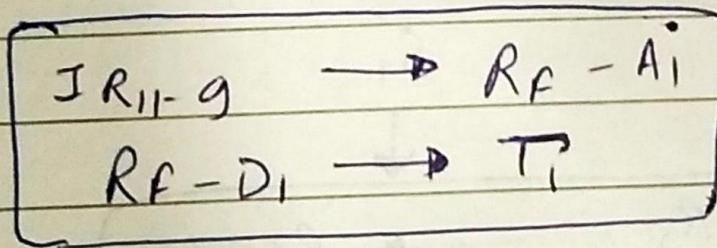



S_{20}

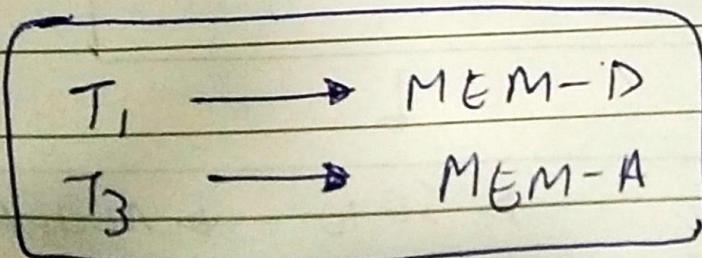

S_{21}

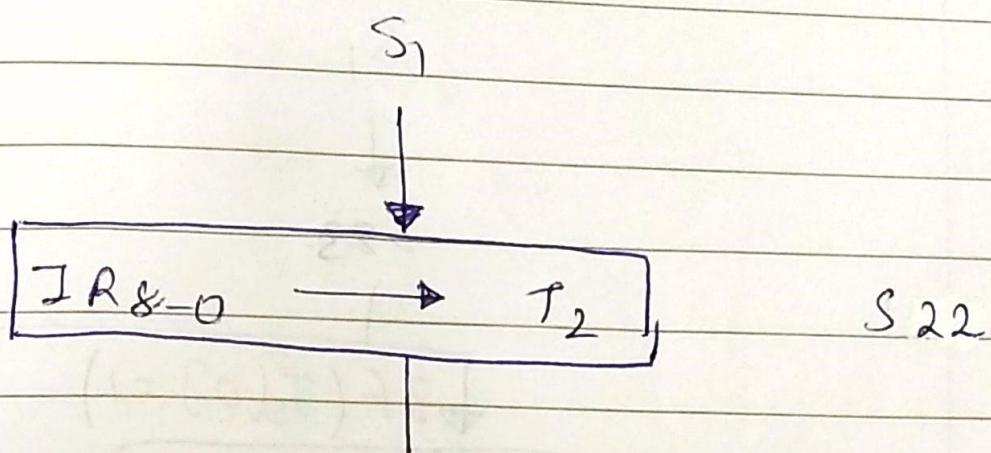11. LM RA, IMM

IF ($T_2[0] = 1$) —

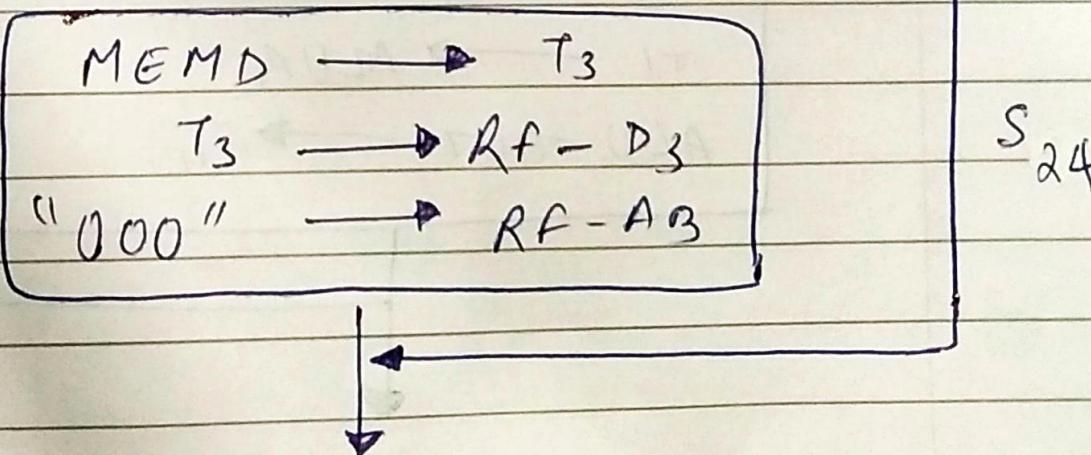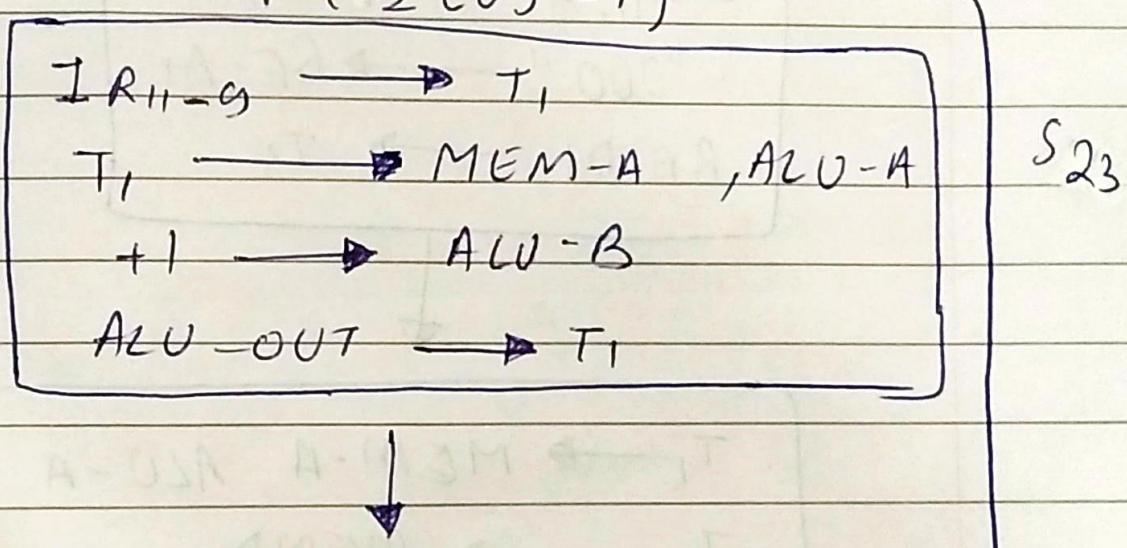


WHILE (VALID NEXT CHECK)



12 SM RA, IMM


Date:

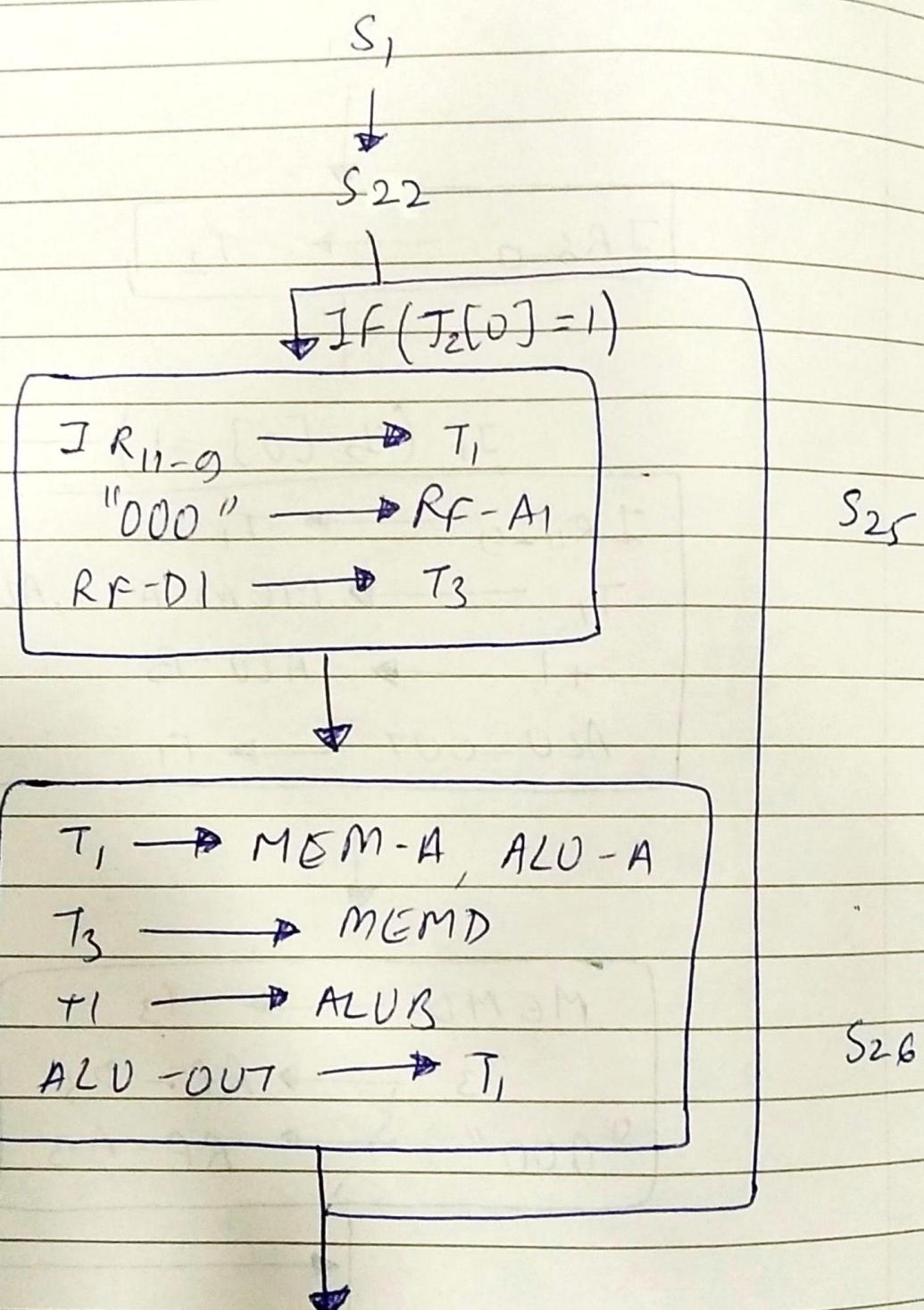


WHILE (VALID NEXT CHECK)

↓
↓
↓

13 BEG , RA , RB , IMM

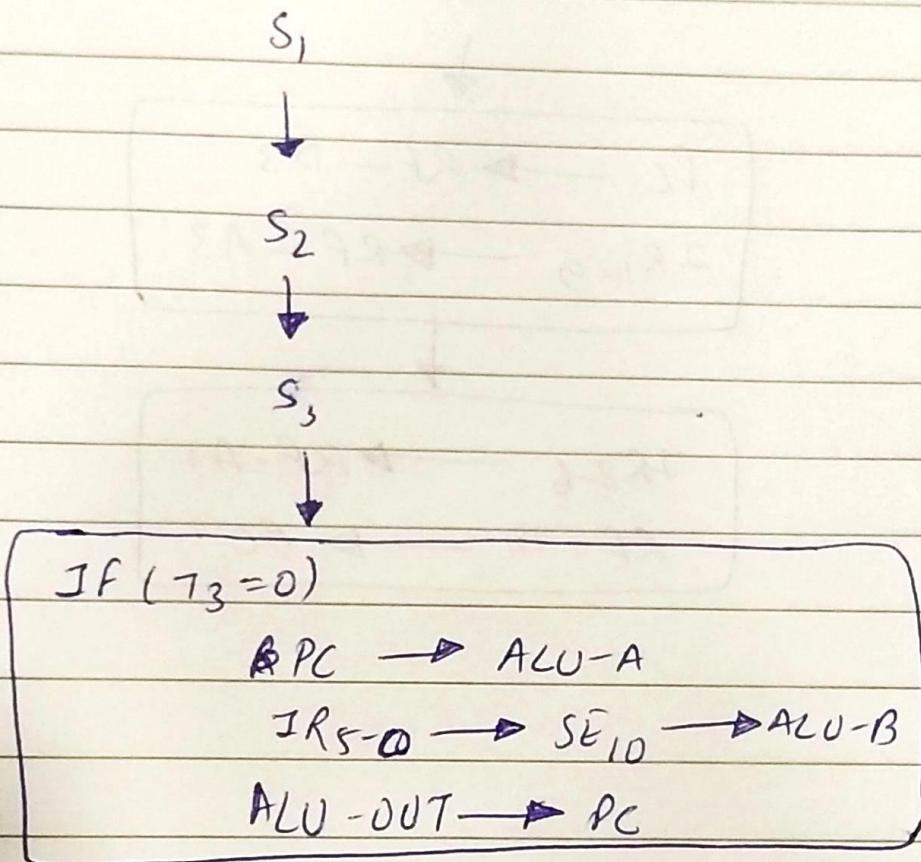
S₂₇

14 JAL RA, IMM

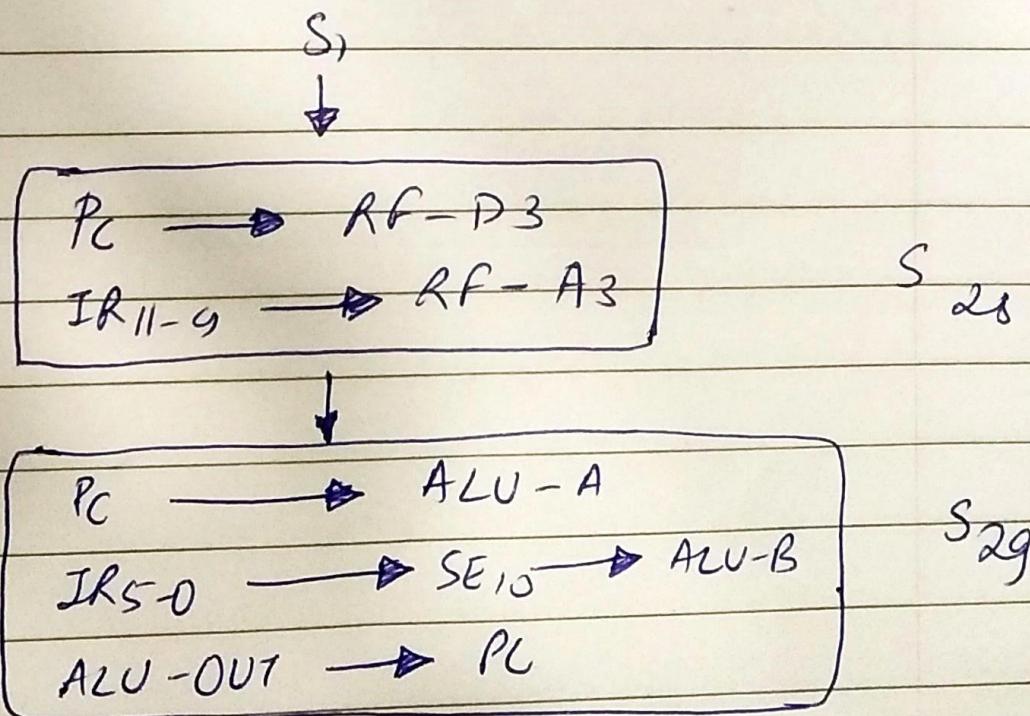
S₂₈S₂₉

15 JLR RA, RB

S₁

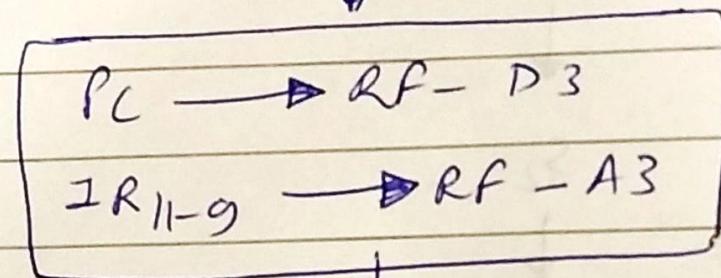

S₂₈

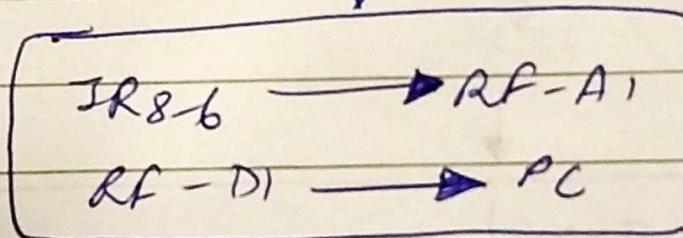

S₃₀

① ALU

The ALU performs basic operations like OR, XOR, AND, etc. by taking two inputs ALU-A & ALU-B of 16 bits each. Its output is represented by ALU-out. The instructions are given directly & multiple control lines are used to control the activities inside ALU.

② Temporary Registers (T_1, T_2, T_3)

Temporary registers store the values for future use. They are all of 16 bits each.

③ MEMORY (MEM)

Memory stores various data at particular locations called addresses. We can access data by providing the address as input (16-bit) through MEM-A & accessing it through MEM-D. We can also store data in memory by providing data to be stored in MEM-D & address in MEM-A.

④ SET, SE10 (SIGN EXTENDER)

The sign extender places the corresponding number of zeroes (7 & 10 resp.) to the left of input so as to make it a 16-bit input.

⑤ REGISTER ALU(RF)

It include all the registers (R_0 to R_7). It has 3 address selection lines (A_1, A_2, A_3) & 3 data output lines D_1, D_2, D_3 . To access a values inside register , we have to pass the address of that register in one of the two address lines A_1 or A_2 . and the corresponding output is selected at D_1/D_2 .

To store a data in a register the data is sent to the D_3 Selection line & the address of the register is sent as input in A_3 .

R_7 register stores the values of Program Counter(PC)

⑥ INSTRUCTION REGISTER (IR)

IR is a special purpose register which is used to receive the 16 bits of instruction. There are three different types of Instruction format (R, I & J type) which allot bits differently to various operands.

Following is the bit distribution-

R-type

$$R_C \rightarrow IR_{5-3}$$

$$R_B \rightarrow TR_{8-6}$$

$$R_A \rightarrow TR_{11-9}$$

I-type

$$IMM \rightarrow TR_{0-5}$$

$$R_B \rightarrow TR_{8-6}$$

$$R_A \rightarrow IR_{n-9}$$

J-type

$$JMM \rightarrow IR_{8-0}$$

$$R_A \rightarrow IR_{11-9}$$

